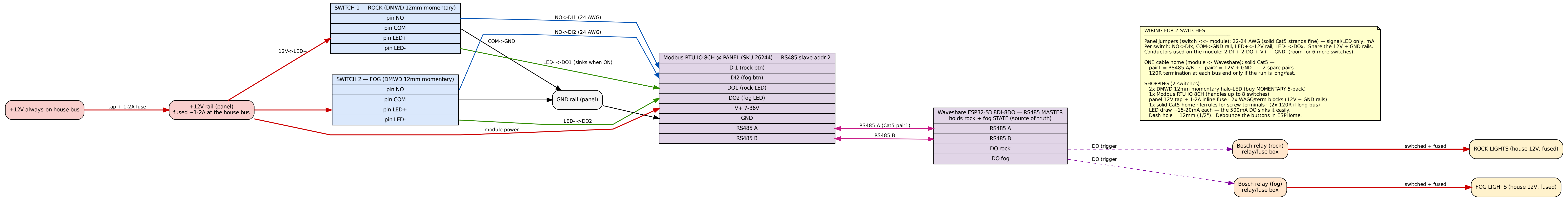


2014 RAM 1500 Carputer — SWITCH PANEL, 2x DMWD 12mm momentary halo-LED buttons (Rock + Fog) on the Modbus IO 8CH  
 Each switch = 4 pins (NO + COM contact, LED+ + LED-). Contact -> a DI (signal only). LED -> a DO (Waveshare drives it = shows true state).  
 LED is 12-24V with a BUILT-IN resistor: LED+ to 12V, LED- to DO, NO external resistor. Verify pin polarity with a meter (markings are tiny).  
 LEGEND: blue = contact->DI · green = LED- ->DO (sink) · red = +12V · black = GND · magenta = RS485 · purple dashed = DO->relay



**WIRING FOR 2 SWITCHES**

Panel jumpers (switch <-> module): 22-24 AWG (solid Cat5 strands fine) — signal/LED only, mA.  
 Per switch: NO->DIx, COM->GND rail, LED+->12V rail, LED- ->DOx. Share the 12V + GND rails.  
 Conductors used on the module: 2 DI + 2 DO + V+ + GND (room for 6 more switches).

ONE cable home (module -> Waveshare): solid Cat5 —  
 pair1 = RS485 A/B · pair2 = 12V + GND · 2 spare pairs.  
 120R termination at each bus end only if the run is long/fast.

SHOPPING (2 switches):  
 2x DMWD 12mm momentary halo-LED (buy MOMENTARY 5-pack)  
 1x Modbus RTU IO 8CH (handles up to 8 switches)  
 panel 12V tap + 1-2A inline fuse · 2x WAGO/term blocks (12V + GND rails)  
 1x solid Cat5 home · ferrules for screw terminals · (2x 120R if long bus)  
 LED draw ~15-20mA each — the 500mA DO sinks it easily.  
 Dash hole = 12mm (1/2"). Debounce the buttons in ESPHome.